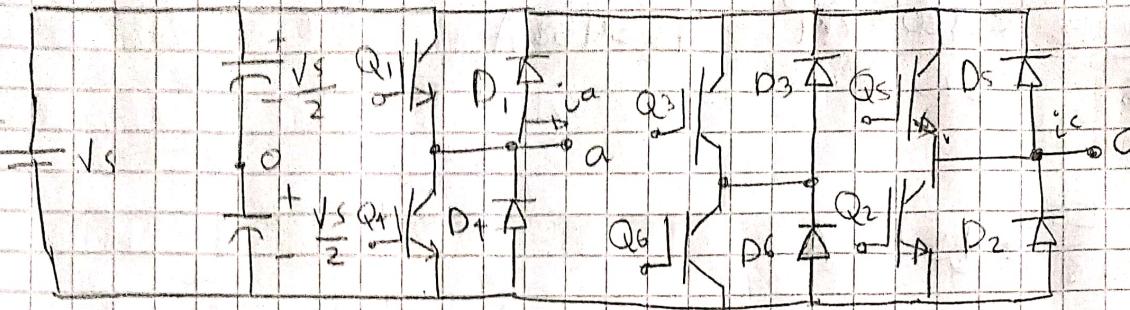


Brian Sebastian Caceres Pinon 1803245

①



$$R = 3\Omega \quad L = 7mH \quad C = 15\mu F \quad f_0 = 400 \text{ Hz} \quad V_s = 220V$$

$$Z_L = j\omega L \quad Z_C = -j \quad Z_n = \frac{-j}{\omega C} \quad Q_n = -Q_{zn}$$

$$Z_n = \sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}$$

$$Q_n = \tan^{-1} \left( \frac{\omega L - \frac{1}{\omega C}}{R} \right)$$

$$I_a = \frac{V_{ab}}{|Z_n|}$$

$$V_{ab} = \sum_{n=1,3,5,7,9,13}^{\infty} \frac{4V_s}{n\pi} \sin\left(\frac{n\pi}{2}\right) \sin\left(\frac{n\pi}{3}\right) \sin\left(n\omega t + \frac{\pi}{6}\right)$$

A)  $V_{ab}(t) = 242,58 \sin(2513,3t + 30^\circ) + -1,1435 \times 10^{-14} \sin(7539,8t + 90^\circ)$   
 $+ -48,517 \sin(12566t + 150^\circ) + 34,655 \sin(17593t + 210^\circ)$   
 $+ 1,1435 \times 10^{-14} \sin(22619t + 270^\circ) + 22,05 \sin(67646t + 330^\circ) [V]$

$$I_a = \frac{V_{ab}}{|Z_n|} [A]$$

$$I_a(t) = 25,74 \sin(2513,3t + 30^\circ) + -2,59 \times 10^{-16} \sin(7539,8t + 90^\circ)  
+ -0,5865 \sin(12566t + 150^\circ) - 0,29025 \sin(17593t + 210^\circ)  
+ 7,3573 \times 10^{-17} \sin(22619t + 270^\circ) + 0,11538 \sin(67646t + 330^\circ) [A]$$

$$I_L = \sqrt{(25,74)^2 + (2,59 \times 10^{-16})^2 + (-0,5865)^2 + (-0,29025)^2 + (7,3573 \times 10^{-17})^2 + (0,11538)^2}$$

$$\sqrt{2}$$

$$I_L = 18,1973 A$$

$$P_L = 3 I_L^2 R = 3 (18,1973)^2 \cdot 3 = 2,9803 \times 10^3 W$$

$$I_s = \frac{P_0}{V_s} = \frac{2,9803 \times 10^3}{220} = 13,5468 \text{ A}$$

$$I_{AVT} = \frac{I_s}{\sqrt{3}} = 4,8156 \text{ A}$$

$$I_{RMS} = \frac{I_s}{\sqrt{3}} = 10,5062 \text{ A}$$

$$THD_{I_a} = \frac{1}{25,74} \sqrt{(-2,59 \times 10^{-6})^2 + (-0,55656)^2 + (-0,20025)^2 + (7,35 \times 10^{-7})^2 + (0,11)^2}$$

$$THD_{I_a} = 0,0258 \Rightarrow 2,58\%$$


$$THD_{V_{ab}} = \frac{1}{242,58} \sqrt{(-1,14 \times 10^{-14})^2 + (-48,51)^2 + (-34,65)^2 + (1,14 \times 10^{-14})^2 + (22,05)^2}$$

$$THD_{V_{ab}} = 0,2621 \Rightarrow 26,21\%$$

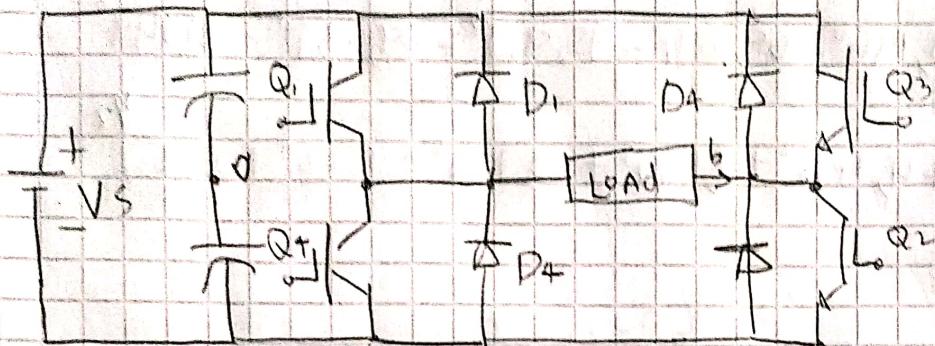(2)

$$R = XL \quad L = 31,5 \text{ mH} \quad C = 112 \text{ nF} \quad f_0 = 60 \text{ Hz}$$

$$\omega = 2\pi f_0 = 316,991 \text{ rad/s}$$



$$X_L = j\omega L = (316,991)(31,5 \text{ m}) j\text{n}$$

$$X_L = 11,875 \text{ jn } \Omega$$

$$X_C = \frac{-j}{\omega C} = \frac{-j}{(316,991)(112 \text{ n})} = -j 23,683/\text{n } \Omega$$

a) Para este tipo de inversor \$V\_o = V\_s\$

$$V_o = V_s = 360 \text{ V}$$

$$b) |z| = [R^2 + (X_L + X_C)^2]^{1/2}$$

$$\text{despejando } R \rightarrow R = [ |z|^2 - (X_L + X_C)^2 ]^{1/2}$$

$$R = [ 23,683^2 - (11,875 - 23,683)^2 ]^{1/2}$$

$$\boxed{R = 20,005 \Omega}$$

$$c) V_o = \sum_{n=1,3,5}^{\infty} \frac{4V_s}{n\pi} \sin(n\omega t)$$

$$V_o = 458,36 \sin(316,9t) + 152,789 \sin(1136,973t) + 91,673 \sin(1884,94t)$$

$$65,481 \sin(2638,937t) + 50,931 \sin(3392,919t) + 41,67 \sin(4146,96t)$$

$$i_o = \frac{V_o}{|z|}$$

$$\text{Don} \quad 19,732 \sin(376,991t) + 4,468 \sin(1130,913t) + 1,576 \sin(1884,956t) \\ + 0,796 \sin(2634,973t) + 0,48 \sin(3397,919t) + 0,32 \sin(4146,901t)$$

$$Q_n = 30,883^\circ - 54,194^\circ + 69,891^\circ - 95,917^\circ - 79,137^\circ - 81,149^\circ$$

$$I_m = (19,732^2 + 4,468^2 + 1,576^2 + 0,796^2 + 0,48^2 + 0,32^2)^{1/2}$$

$$I_m = 20,316 \text{ A}$$

$$I_0 = \frac{I_m}{\sqrt{2}} = 14,365 \text{ A.}$$

$$P_0 = \frac{V_0^2 \cdot 360^2}{R} = \boxed{6480 \text{ W}}$$

$$\text{d) } I_{sp} = I_m = \boxed{20,316 \text{ A.}}$$

③ Discreto Control UPWM RMS out 70% mudi: no

→ Para el UPWM se define el número de pulsos necesarios

$$P = \frac{M_f}{2}$$

$$M_f = \frac{f_c}{f_0}$$

2 pulsos por ciclo.

$$M_f = 2 \text{ y } P = 1$$



Frecuencia del inversor a 400 Hz

$$f_c = 2 \cdot 400 = 800 \text{ Hz}$$

(3)

$$\textcircled{a} \quad \frac{4 \text{ Vs}}{\sqrt{2} \pi} \sin\left(\frac{\delta}{2}\right) = V_{\text{rms}} = 0,7 \text{ Vs}$$

$$\delta = 102,06^\circ$$

$$360 \text{ V}_{\text{rms}} = 0,9 \text{ Vs}$$

$$\text{Vs} = 400 \text{ V}$$

(b)

$$M \left( \frac{A_r}{A_{cr}} \right) = \frac{8 \cdot 2P}{WT} = \frac{102,06^\circ \left( \frac{\pi}{180^\circ} \right) (2)(1)}{(60) 2\pi \frac{1}{60}}$$

$$M \left( \frac{A_r}{A_{cr}} \right) = 0,56$$

$$\textcircled{c} \quad f_p = P \cdot 2 \cdot f = (1)(2)(60) = 120 \text{ Hz}$$

(d)

$$A_{cr} = Sv$$

$$M = \frac{A_r}{A_{cr}}$$

$$A_r = A_{cr} \cdot M = 0,56 \cdot Sv$$

$$A_r = 2,91 \text{ V}$$